

Cvičenie 6

Čítače vo VHDL, Hierarchický dizajn, Úvod do skriptov pre ModelSIM

Zadanie:

Realizujte parametrizovateľný čítač na doske CPLD_KIT, tak by výstup čítača bol zobrazený na 7 segmentovom displeji. Parametre majú byť: frekvencia pričítavania, horný limit v rozsahu 1 až 15 a krok pričítavania v rozsahu 1 až 5. Popis celého čítača realizujte hierarchicky, teda zvlášť popis: parametrizovateľnej deličky, samotného čítača a dekóderu. Signály medzi uvedenými popismi poprepájajte v rámci popisu „Top Level“ entity. Projekt odsimulujte v ModelSIMe tak, aby boli zobrazené nielen signály z Test benchu, ale aj interné signály z „Top Level“ entity. Projekt nahrajte do adresára BASIC_CNT, a nazvite ho BASIC_CNT !!!

Riešenie:

Výklad k celému projektu bude uskutočnený na cvičení a základná filozofia hierarchického dizajnu je naznačená na obrázku na 2. strane. V rámci tohto dokumentu budú uvedené zdrojové kódy a postup ako do dizajnu zakomponovať jednoduchý konfiguračný skript pre ModelSIM, ktorý do výstupného grafického okna vloží požadované priebehy signálov a nastaví sa v ňom konečný čas simulácie.

Výpis konfiguračného skriptu pre ModelSIM: waves.do


(Pre celkové nastavenie simulácie tento skript nestačí. Viac sa o týchto skriptoch dozviete na nasledujúcich cvičeniach. V skutočnosti QUARTUS II generuje ešte jeden .do súbor, (napr: BASIC_CNT_run_msim_rtl_vhdl.do pre funkčnú simuláciu), v ktorom sú zvyšné nastavenia simulácie)

waves.do:


```
#adding waves
add wave sim:/stim_basic_cnt/clk50mhz_stim
add wave sim:/stim_basic_cnt/reset_stim
add wave sim:/stim_basic_cnt/display_stim
add wave sim:/stim_basic_cnt/the_basic_cnt/clk
add wave sim:/stim_basic_cnt/the_basic_cnt/bcdcnt
 
#setting running time
run 10us
```

Nastavenie v QUARTUS II: horné menu>Assignments>EDA Tool Settings>Simulation
(zafajknút' Use script to set up simulation: a nabrowsovať waves.do)



 Znázormenie usporiadania a logického poprepájania súborov projektu z hľadiska syntézy a simulácie.



BASIC_CNT.vhd:

```
library ieee;
use ieee.std_logic_1164.all;

entity BASIC_CNT is
port(
    CLK50MHZ      : in std_logic;
    RESET         : in std_logic;
    DISPLAY        : out std_logic_vector(7 downto 0)
);
end BASIC_CNT;

architecture arch of BASIC_CNT is

constant DIV_FACTOR      : natural range 1 to 25000000 := 5;
constant LIMIT            : natural range 1 to 15          := 12;
constant INCREMENT        : natural range 1 to 5           := 2;

signal clk                : std_logic;
signal bcdcnt             : std_logic_vector(3 downto 0);

component PRESCALER is
generic(
    DIV_FACTOR : natural range 1 to 25000000 := 10
);
port(
    CLK50MHZ      : in std_logic;
    RESET         : in std_logic;
    CLKOUT        : out std_logic
);
end component;

component COUNTER is
generic(
    LIMIT        : natural range 1 to 15 := 10;
    INCREMENT    : natural range 1 to 5  := 1
);
port(
    CLK          : in std_logic;
    RESET        : in std_logic;
    CNTOUT       : out std_logic_vector(3 downto 0)
);
end component;

component BCD2SEG is
port(
    BCDIN        : in std_logic_vector (3 downto 0);
    DISPLAY       : out std_logic_vector (7 downto 0)
);
end component;

begin

the_PRESCALER: PRESCALER
generic map(
    DIV_FACTOR => DIV_FACTOR
)
port map(
    CLK50MHZ    => CLK50MHZ,
    RESET        => RESET,
    CLKOUT       => clk
);

the_COUNTER: COUNTER
generic map(
    LIMIT        => LIMIT,
```

```

        INCREMENT  => INCREMENT
    )
port map(
    CLK          => clk,
    RESET       => RESET,
    CNTOUT      => bcdcnt
);

the_BCD2SEG: BCD2SEG
port map(
    BCDIN       => bcdcnt,
    DISPLAY     => DISPLAY
);

end arch;

```

PRESCALER.vhd:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all; -- using comparison "<"

entity PRESCALER is
    generic(
        DIV_FACTOR : natural range 1 to 25000000 := 10
    );
    port(
        CLK50MHZ    : in std_logic;
        RESET       : in std_logic;
        CLKOUT      : out std_logic
    );
end PRESCALER;

architecture arch of PRESCALER is

    signal cnt : std_logic_vector (24 downto 0);
    signal clk : std_logic;

begin
    CLKOUT <= clk;

    process(RESET,CLK50MHZ)
    begin
        if (RESET = '0') then
            cnt <= (others => '0');
            clk <= '0';
        elsif (rising_edge(CLK50MHZ)) then
            if (cnt < DIV_FACTOR/2) then
                cnt <= cnt + 1;
            else
                cnt <= (others => '0');
                clk <= not clk;
            end if;
        end if;
    end process;
end arch;

```

COUNTER.vhd:

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all; -- using comparison "<"

entity COUNTER is
    generic(

```

```

LIMIT      : natural range 1 to 15 := 10;
INCREMENT  : natural range 1 to 5  := 1
);
port(
  CLK       : in std_logic;
  RESET     : in std_logic;
  CNTOUT    : out std_logic_vector(3 downto 0)
);
end COUNTER;

architecture arch of COUNTER is

  signal cnt : std_logic_vector (3 downto 0);

begin

  CNTOUT <= cnt;

  process(RESET,CLK)
  begin
    if (RESET = '0') then
      cnt <= (others => '0');
    elsif (rising_edge(CLK)) then
      if (cnt < LIMIT) then
        cnt <= cnt + INCREMENT;
      else
        cnt <= (others => '0');
      end if;
    end if;
  end process;
end arch;

```

BCD2SEG.vhd:

```

library ieee;
use ieee.std_logic_1164.all;

entity BCD2SEG is
  port(
    BCDIN   : in std_logic_vector (3 downto 0);
    DISPLAY : out std_logic_vector (7 downto 0)
  );
end BCD2SEG;

architecture arch of BCD2SEG is
begin
  with BCDIN select
    DISPLAY <=
      "00000001" when "0000", -- 0
      "10011111" when "0001", -- 1
      "00100101" when "0010", -- 2
      "00001101" when "0011", -- 3
      "10011001" when "0100", -- 4
      "01001001" when "0101", -- 5
      "01000001" when "0110", -- 6
      "00011111" when "0111", -- 7
      "00000001" when "1000", -- 8
      "00001001" when "1001", -- 9
      "00010001" when "1010", -- A
      "11000001" when "1011", -- b
      "11100101" when "1100", -- c
      "10000101" when "1101", -- d
      "01100001" when "1110", -- E
      "01110001" when "1111", -- F
      "11111111" when others; -- pre ine moznosti
end arch;

```

stim_BASIC_CNT.vhd

(nezabudnite nastavíť vlastnosti tohto súboru ako „VHDL Test Bench File“)

```
library ieee;
use ieee.std_logic_1164.all;

entity stim_BASIC_CNT is
end stim_BASIC_CNT;

architecture stim of stim_BASIC_CNT is

component BASIC_CNT is
port(
    CLK50MHZ      : in std_logic;
    RESET         : in std_logic;
    DISPLAY       : out std_logic_vector(7 downto 0)
);
end component;

constant TIME_PERIOD : time := 20ns;

signal CLK50MHZ_stim, RESET_stim : std_logic := '0';
signal DISPLAY_stim             : std_logic_vector(7 downto 0);

begin

the_BASIC_CNT: BASIC_CNT
    port map (
        CLK50MHZ => CLK50MHZ_stim,
        RESET      => RESET_stim,
        DISPLAY    => DISPLAY_stim
    );

-- generating the 50MHz Clock signal
CLK50MHZ_stim <= not CLK50MHZ_stim after TIME_PERIOD/2;

-- hold reset for 4 clock cycles_
stimulus: process
begin
    RESET_stim <= '0';
    wait for TIME_PERIOD*4;
    RESET_stim <= '1';
    wait;
end process stimulus;

end stim;
```