


Voltage and current measurement - multimeters

DC voltage measurement

- Typical DC voltage to be measured: 1mV – 100VDC – common multimeters
- Out of our scope:
 - Small DC voltage (μV or nV): difficult (voltage offset and drift of DC amplifiers), special nano and microvoltmeters
 - High voltage (above kV) – question of user safety, isolation materials – special high voltage probes, indirect measurements
- **DC voltmeter and DC voltage measurement is the basic function of nearly all modern digital multimeters**
 - At other quantities to be measured are converted to DC voltage inside multimeters


2

Measuring DCV

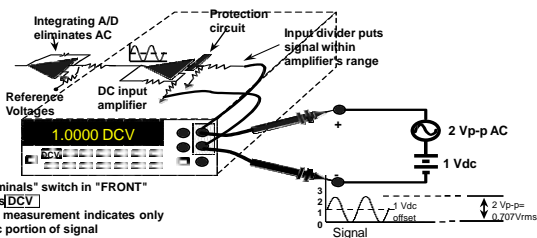


**Terminals* switch in "FRONT"
 *Press [DCV]
 *Note measurement indicates only the dc portion of signal

Connection

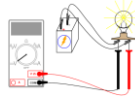

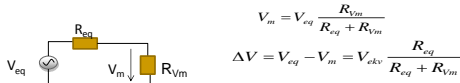- Voltmeter must be connected in parallel
- The input resistance (impedance) must be much higher than internal equivalent resistance (impedance) in measured points to decrease the measurement error ΔV
 - modern digital multimeters $R_{\text{voltmeter}} \sim 10 - 100M\Omega$





$$V_m = V_{eq} \frac{R_{vm}}{R_{eq} + R_{vm}}$$

$$\Delta V = V_{eq} - V_m = V_{eq} \frac{R_{eq}}{R_{eq} + R_{vm}}$$

4

Leads connection

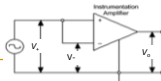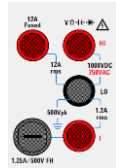- Hi, Lo/com – voltage is measured between them
- Voltage / current inputs (connectors for leads)
- **Be careful of common voltage!**
 - CMV – the voltage among inputs and general ground.
 - Overloading the given limit can destroy the instrument
 - Common mode ration (CMR in dB) – rejection of common voltage on result of measurement




5

Basic electronic circuits

$$V_{out} = G(V_1 - V_2)$$

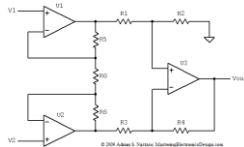- Instrumentation amplifiers
 - High input resistance
 - Easy gain control by one resistor R_G
 - Low f_{max}
- AD conversion
 - High resolution (number of bits)
 - Low rate of measurements
 - Integrating ADC
 - Sigma-delta or successive approximation followed by digital processing



$$V_{DC} = \frac{1}{N} \sum_{t=1}^N V(t_t)$$

6


AC voltage measurement

- Required parameter of AC voltage to be measured: rms value
 - AC voltage is converted to DC voltage
 - Rectifiers
 - Convertors to rms
- Bandwidth:
 - multimeter: Hz – kHz (see datasheet)
 - Special AC voltmeters – narrowband (out of scope)
- Is DC component included into measurement?

$$V_{rms\ ac+dc} = \sqrt{\frac{1}{T} \int_0^T v_{ac+dc}^2(t) dt} = \sqrt{\frac{1}{T} \int_0^T V_{dc}^2 dt + \frac{1}{T} \int_0^T v_{ac}^2(t) dt} = \sqrt{V_{dc}^2 + V_{rms\ ac}^2}$$


7

Measuring ACV

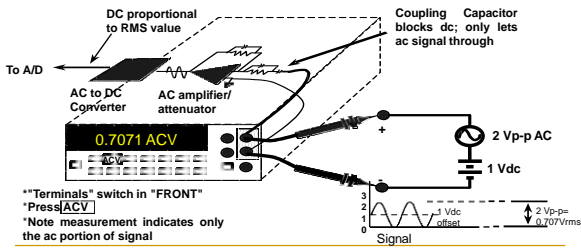

Conversion AC to DC

- Rectifiers
 - Passive
 - Active

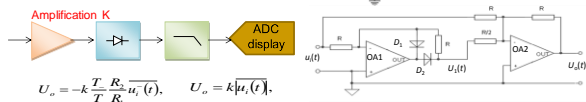

- Output DC is not rms value of input AC voltage!!!

9

Is it possible to recalculate the mean of absolute value to rms value?

■ Harmonic

$$U_m = \text{avr}\{A \sin(2\pi f t)\} = \frac{1}{\pi} \int_0^\pi A \sin(x) dx = \frac{A}{\pi} [-\cos x]_0^\pi = \frac{2A}{\pi}$$

$$U_{rms} = \frac{A}{\sqrt{2}} \Rightarrow K = \frac{U_m}{U_{rms}} = \frac{\pi}{2\sqrt{2}}$$

■ Triangular

$$U_m = \text{avr}\left\{\frac{A}{\sqrt{2}}\right\} = \frac{1}{T} \int_0^T \frac{2At}{\sqrt{2}} dt = \frac{4A}{T^2} \left[\frac{t^2}{2}\right]_0^T = \frac{2A}{\sqrt{2}}$$

$$U_{rms} = \frac{A}{\sqrt{3}} \Rightarrow K = \frac{U_m}{U_{rms}} = \frac{2}{\sqrt{3}}$$


■ Square

$$U_m = \text{avr}\{A\} = \frac{1}{T} \int_0^T A dt = \frac{2A}{T} \left[\frac{t}{2}\right]_0^T = A$$

$$U_{rms} = A \Rightarrow K = \frac{U_m}{U_{rms}} = 1$$

10

RMS value?

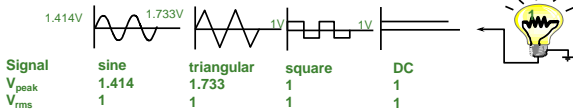

- The ratio rms value / mean value or peak value (achieved by rectification) = shape coefficient is not constant (it depends on waveform shape)
- AC voltmeter with rectifier is calibrated for sinewave to indicate rms value; the indicated value is wrong for different shapes

11

Converters to the TRUE rms


■ Definition contains nonlinear operations

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T v_{ic}^2(t) dt}$$


- Nonlinear circuits – difficult to keep stable parameters (nonlinearity) during long period

■ Solutions

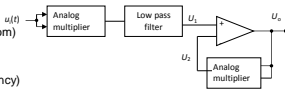- Analog processing (see e.g. www.analog.com)
 - Explicit principle
 - Implicit principle
 - Conversion on temperature (high frequency)
 - ...



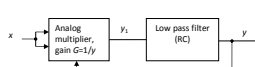- Digital processing
 - Calculation from digitized signal




$$V_{RMS} = \sqrt{\frac{1}{N} \sum_{i=1}^N v^2(iT_s)}$$

12

Crest factor

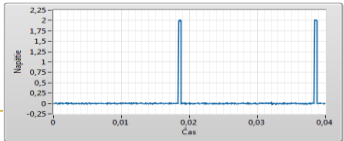- **Crest factor** of signal is defined as the ratio of peak value to rms value of a waveform
- It describes for AC voltmeter the maximal overloading of instrument without limitation of measured signal
- Example of signal




Current measurement

- Ammeter
- The common need and ranges from μA to tens A
- Difficulties:
 - Small DC current (nA or pA) – input current and its drift
 - Large currents above 100A – indirect methods based on EM field, ...
- **Multimeter in the mode of ammeter: conversion from current to voltage in multimeter input circuits**


14

Measuring CURRENT

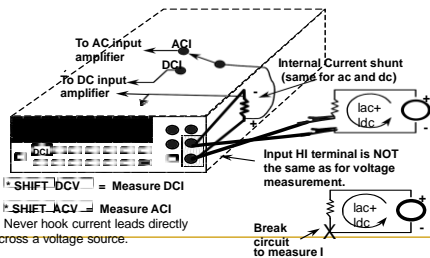

Connection

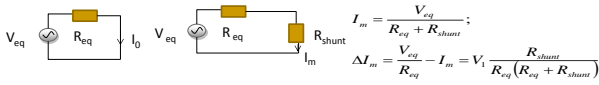
- Ammeter must be connected into break of circuit
- Input resistance (shunt) changes conditions in the measured circuit – the results of measurement differs from true current in circuit without meter (systematic error)
- The smaller is the input resistance the smaller is the error – modern digital multimeters $R_{ampmeter} \sim 0,1 - 10\Omega$



16

Conversion I to V

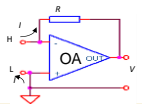
- Very small resistance
- Passive converters = accurate sensing resistor – shunt
 - Conversion constant is given by resistance of shunt
- Active (electronic) converters with operational amplifier
 - $V = -R \cdot I$



17

Large current measurement

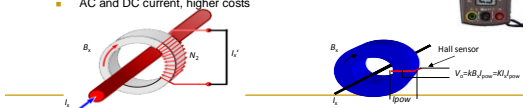
- Clamp meters
- Two principles:
 - Current transformer:
 - Only AC current, limited bandwidth
 - Low cost, simple construction
 - Hall sensor – semiconductor sensor of magnetic field:
 - AC and DC current, higher costs



18


DC resistance measurement

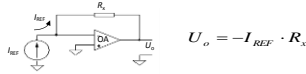- Test signal: DC current
 - Principle based on Ohm law – measuring voltage across the measured resistor at known current
- $$R_x = \frac{V_{measured}}{I_{source}}$$
- Modern instrumentations: active convertor resistance to voltage




19

Measuring Resistance, Two-Wire Technique

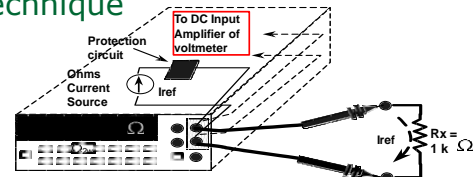

- **Terminals" switch in "FRONT"
- *Press [2W]
- *Since voltage is sensed at front terminals, measurement includes all lead resistance
- * To eliminate the lead resistance:
 - * Short leads together
 - * Press [Null]
 - * Original value will now be subtracted from each reading

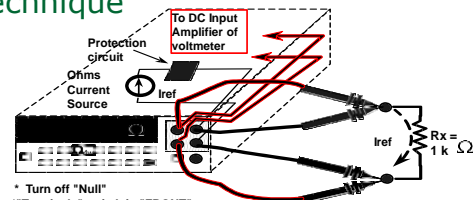
Measuring Resistance - Four-Wire Technique



- * Turn off "Null"
- **Terminals" switch in "FRONT"
- *Press [4W]
- *Voltage is now sensed directly at the resistor, so lead resistance is not a factor
- * Because input impedance of DC Input Amplifier is so high, no current flows through sense leads, hence no lead resistance error

Measuring capacity and inductance

- Conversion C or L to DC voltage

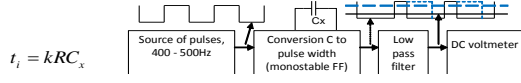

$$t_i = kRC_x$$


$$U_m = U_H \frac{t_i}{T} + U_L \frac{T-t_i}{T} = (U_H - U_L) \frac{t_i}{T} + U_L = (U_H - U_L) \frac{kRC_x}{T} + U_L$$

$$C_x = \frac{U_m - U_L}{U_H - U_L} \frac{T}{kR} = aU_m + b \quad \text{if } U_L = 0 \quad C_x = \frac{U_m}{U_H} \frac{T}{kR} = KU_m$$

22

Diode and bipolar transistor test


- Diode:
 - PN junction test by constant DC current
 - If junction is open, the voltage across the junction is indicated
 - If junction is closed (reverse direction), the meter indicates overload
 - Results indicate anode and cathode terminal and status of PN junction (broken)
- Bipolar transistor
 - Test of BC and BE junctions (diodes – status, NPN or PNP)
 - Common-emitter current gain h_{21E} (β_E)

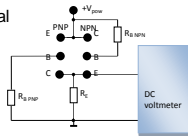

23

Block diagram

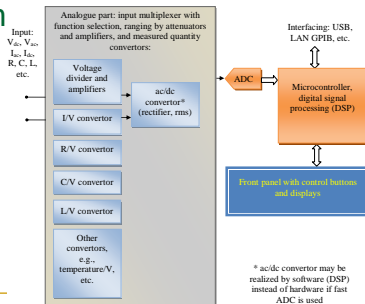- Many measuring functions
- Conversion of any measured quantity to DC voltage
- Additional functions:
 - Statistical data processing
 - Communication interface
 - Continuity test
 - Triggering
 - Additional displays with numerical and graphical presentation of acquired results



* ac/dc converter may be realized by software (DSP) instead of hardware if fast ADC is used

Examples

- Handheld (batteries)
- Desktop (socket 230V)



25
