


## Cvičenie 8

### Konečné automaty – Doplňok k Cvičeniu 7


#### Popis:

Kód bol formálne upravený (pre účely štúdia používajte túto verziu kódu),  
Bola pridaná hierarchická schéma,  
Bol pridaný stavový diagram.

#### Hierarchická schéma:

 

## Stavový diagram:

 

## STATE\_DEMO.vhd (top-entity)

```
library ieee;
use ieee.std_logic_1164.all;

entity STATE_DEMO is
port(
    CLK50MHZ      : in std_logic;
    RESET         : in std_logic;
    DISPLAY1      : out std_logic_vector(7 downto 0);
    DISPLAY10     : out std_logic_vector(7 downto 0);
    START_BUT     : in std_logic;
    SET_BUT       : in std_logic;
    SET_SWICH     : in std_logic_vector(2 downto 0);
    BUZZER_PLUS   : out std_logic;
    BUZZER_MINUS  : out std_logic
);

end STATE_DEMO;

architecture arch of STATE_DEMO is

constant DIV_FACTOR_SM  : natural range 100000 to 25000000 := 2500000;
constant DIV_FACTOR_BUZ : natural range 1000    to 100000   := 50000;

signal clk_sm          : std_logic;
signal clk_buzzer       : std_logic;
signal bcdcnt1         : std_logic_vector(3 downto 0);
signal bcdcnt10        : std_logic_vector(3 downto 0);
signal buzzer_enable   : std_logic;

component PRESCALER is
generic(
    DIV_FACTOR_SM  : natural range 100000 to 25000000 := 2500000;
    DIV_FACTOR_BUZ : natural range 1000    to 100000   := 50000
);
port(
    CLK50MHZ      : in std_logic;
    RESET         : in std_logic;
    CLKOUT1       : out std_logic;
    CLKOUT2       : out std_logic
);
end component;

component SM is
port(
    CLK           : in std_logic;
    RESET         : in std_logic;
    CNTOUT1      : out std_logic_vector(3 downto 0);
    CNTOUT10     : out std_logic_vector(3 downto 0);
    START_BUT    : in std_logic;
    SET_BUT      : in std_logic;
    SET_SWICH    : in std_logic_vector(2 downto 0);
    BUZZER_EN    : out std_logic
);
end component;

component BCD2SEG is
port(
    BCDIN        : in std_logic_vector (3 downto 0);
    DISPLAY      : out std_logic_vector (7 downto 0)
);
end component;

component BUZZER is
port(
    CLK_DRIVE    : in std_logic;
    ENABLE       : in std_logic;
    OUT_PLUS    : out std_logic;
    OUT_MINUS   : out std_logic
);
end component;
```

```

begin

    the_PRESCALER: PRESCALER
        generic map(
            DIV_FACTOR_SM  => DIV_FACTOR_SM,
            DIV_FACTOR_BUZ => DIV_FACTOR_BUZ
        )
        port map(
            CLK50MHZ      => CLK50MHZ,
            RESET         => RESET,
            CLKOUT1       => clk_buzzer,
            CLKOUT2       => clk_sm
        );

    the_SM: SM
        port map(
            CLK          => clk_sm,
            RESET        => RESET,
            CNTOUT1     => bcdcnt1,
            CNTOUT10    => bcdcnt10,
            START_BUT   => START_BUT,
            SET_BUT     => SET_BUT,
            SET_SWICH   => SET_SWICH,
            BUZZER_EN   => buzzer_enable
        );

    the_BCD2SEG1: BCD2SEG
        port map(
            BCDIN        => bcdcnt1,
            DISPLAY      => DISPLAY1
        );

    the_BCD2SEG10: BCD2SEG
        port map(
            BCDIN        => bcdcnt10,
            DISPLAY      => DISPLAY10
        );

    the_BUZZER: BUZZER
        port map(
            CLK_DRIVE   => clk_buzzer,
            ENABLE      => buzzer_enable,
            OUT_PLUS    => BUZZER_PLUS,
            OUT_MINUS   => BUZZER_MINUS
        );
end arch;

```

**SM.vhd**

```

-- konecny automat
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all; -- using comparison "<"

entity SM is
    port(
        CLK          : in std_logic;                      -- hodiny
        RESET        : in std_logic;                      -- reset
        CNTOUT1     : out std_logic_vector(3 downto 0); -- vystup citaca jednotiek
        CNTOUT10    : out std_logic_vector(3 downto 0); -- vystup citaca desiatok
        START_BUT   : in std_logic;                       -- tlacidlo pre start
        SET_BUT     : in std_logic;                       -- prepinac rezimu:
        odpocitavanie/nastavenie pociatocnej hodnoty
        SET_SWICH   : in std_logic_vector(2 downto 0); -- swich na nastavenie
        pociatocnej hodnoty
        BUZZER_EN   : out std_logic;                     -- aktivacia bzuciaku
    );
end SM;

architecture arch of SM is

type my_state is (wait_for_start, refresh, run_down, set_time, finish);

```

```

signal cnt1      : std_logic_vector (3 downto 0); -- citac jednotiek
signal cnt10     : std_logic_vector (2 downto 0); -- citac desiatok
signal cnt10_preset : std_logic_vector (2 downto 0); -- prednastavenie desiatok
signal cnt_finish : std_logic_vector (3 downto 0); -- citac, ktorý zabezpecuje
prerusovany ton
signal state      : my_state;                      -- konecny automat

begin

  CNTOUT1 <= cnt1;
  CNTOUT10 <= '0' & cnt10;
  BUZZER_EN <= '1' when ((state = finish) and (cnt_finish(0) = '1')) else '0';

process(RESET,CLK)
begin
  if (RESET = '0') then                         -- nastavenie hodnot po resete
    cnt1 <= (others => '0');
    cnt10 <= "111";
    cnt10_preset <= "111";
    state <= wait_for_start;
    cnt_finish <= (others => '1');
  elsif (rising_edge(CLK)) then

    case state is
      when wait_for_start =>                  -- cakanie na start od pocitavania alebo
        if (SET_BUT = '0') then                -- nastavenie pociatocnej hodnoty
          state <= set_time;
        elsif (START_BUT = '0') then
          state <= run_down;
        else
          state <= wait_for_start;
        end if;

      when run_down =>                      -- od pocitavanie
        if (cnt1 /= 0) then                  -- od pocitavanie jednotiek po nulu
          cnt1 <= cnt1 - 1;
        else                                -- nastavenie jednotiek na 9
          cnt1 <= "1001";
          if(cnt10 /= 0) then               -- od pocitanie desiatky po nulu
            cnt10 <= cnt10 - 1;
          else
            cnt10 <= "000";
            cnt1 <= "0000";
            state <= finish;              -- ak sa jednotky aj desiatky rovnaju 0
            end if;
          end if;

      when finish =>                      -- generovanie prerusovaneho tonu
        if (cnt_finish /= 0) then
          cnt_finish <= cnt_finish - 1;   -- casove oneskorenie, pocas ktorého
        else                                -- zaznie zvukovy signal
          state <= refresh;
        end if;

      when refresh =>                    -- nacitanie pociatocnej hodnoty
        cnt10 <= cnt10_preset;
        cnt1 <= "0000";
        state <= wait_for_start;
        cnt_finish <= (others => '1');

      when set_time =>                  -- rezim nastavenia pociatocnej hodnoty
        cnt10 <= not SET_SWITCH;
        cnt10_preset <= not SET_SWITCH;
        cnt1 <= "0000";
        if (SET_BUT = '1') then
          state <= wait_for_start;
        end if;

    end case;

  end if;
end process;

```

```

end arch;

PRESALER.vhd
-- presaler
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all; -- using comparison ""<"""

entity PRESALER is
  generic(
    DIV_FACTOR_SM : natural range 100000 to 25000000 := 2500000;
    DIV_FACTOR_BUZ : natural range 1000 to 100000 := 50000
  );
  port(
    CLK50MHZ : in std_logic;
    RESET : in std_logic;
    CLKOUT1 : out std_logic;
    CLKOUT2 : out std_logic
  );
end PRESALER;

architecture arch of PRESALER is

  signal cnt1 : std_logic_vector (24 downto 0);
  signal cnt2 : std_logic_vector (24 downto 0);
  signal clk1 : std_logic;
  signal clk2 : std_logic;

begin
  CLKOUT1 <= clk1;
  CLKOUT2 <= clk2;

  process(RESET,CLK50MHZ)
  begin
    if (RESET = '0') then
      cnt1 <= (others => '0');
      cnt2 <= (others => '0');
      clk1 <= '0';
      clk2 <= '0';
    elsif (rising_edge(CLK50MHZ)) then
      if (cnt1 < DIV_FACTOR_BUZ/2) then
        cnt1 <= cnt1 + 1;
      else
        cnt1 <= (others => '0');
        clk1 <= not clk1;
        if (cnt2 < DIV_FACTOR_SM/DIV_FACTOR_BUZ) then
          cnt2 <= cnt2 + 1;
        else
          cnt2 <= (others => '0');
          clk2 <= not clk2;
        end if;
      end if;
    end if;
  end process;
end arch;

```

```

BCD2SEG.vhd
-- decoder
library ieee;
use ieee.std_logic_1164.all;

entity BCD2SEG is
  port(
    BCDIN : in std_logic_vector (3 downto 0);
    DISPLAY : out std_logic_vector (7 downto 0)
  );
end BCD2SEG;

architecture arch of BCD2SEG is
begin
  with BCDIN select
    DISPLAY <=

```

```

"00000011" when "0000", -- 0
"10011111" when "0001", -- 1
"00100101" when "0010", -- 2
"00001101" when "0011", -- 3
"10011001" when "0100", -- 4
"01001001" when "0101", -- 5
"01000001" when "0110", -- 6
"00011111" when "0111", -- 7
"00000001" when "1000", -- 8
"00001001" when "1001", -- 9
"00010001" when "1010", -- A
"11000001" when "1011", -- b
"11100101" when "1100", -- c
"10000101" when "1101", -- d
"01100001" when "1110", -- E
"01110001" when "1111", -- F
"11111111" when others; -- pre ine moznosti
end arch;

```

### **BUZZER.vhd**

```

-- buzzer
library ieee;
use ieee.std_logic_1164.all;

entity BUZZER is
  port(
    CLK_DRIVE      : in std_logic;
    ENABLE         : in std_logic;
    OUT_PLUS       : out std_logic;
    OUT_MINUS      : out std_logic
  );
end BUZZER;

architecture arch of BUZZER is

begin

  OUT_PLUS  <= CLK_DRIVE when (ENABLE = '1') else '0';
  OUT_MINUS <= not CLK_DRIVE when (ENABLE = '1') else '1';

end arch;

```

## Priradenie pinov:

